
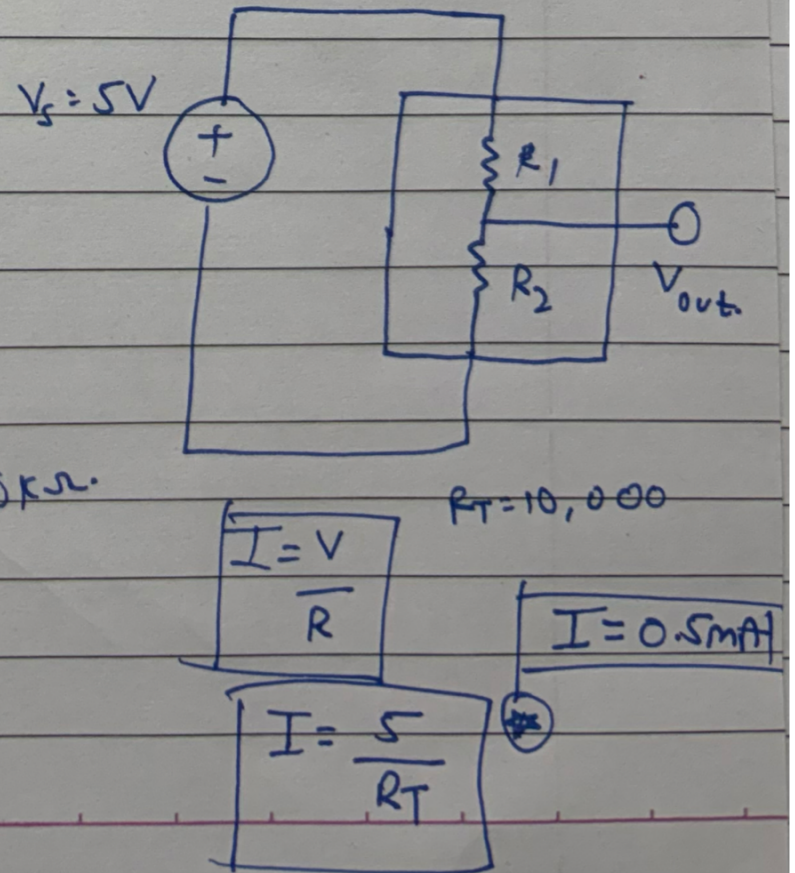


Potentiometer

- Device used to vary resistance.

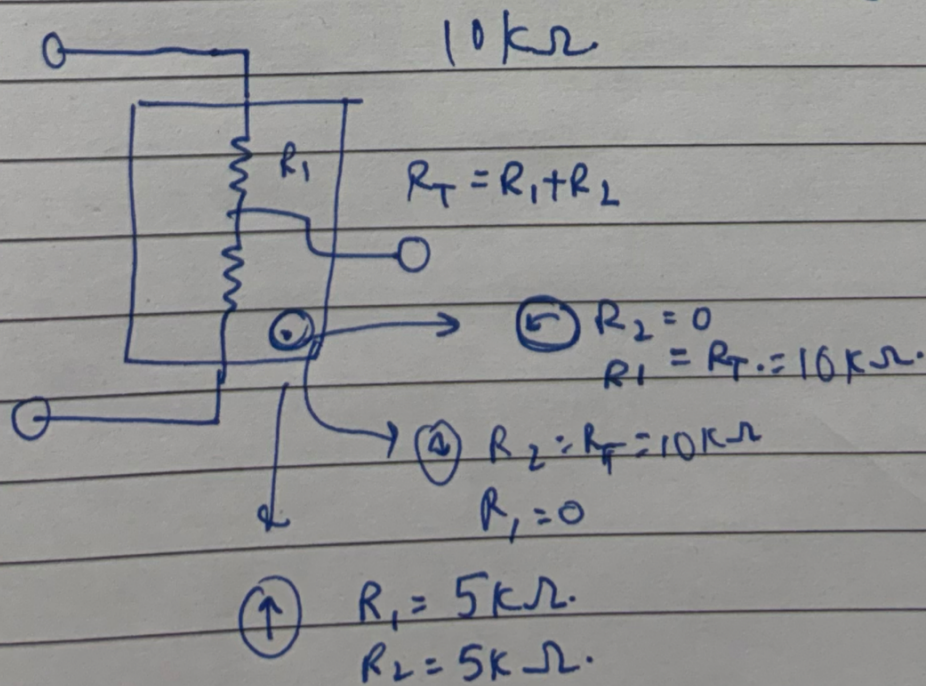

$$V_{out} = I \times R_2.$$

$$V_{out} = 0.5 \text{ mA} \times R_2$$