

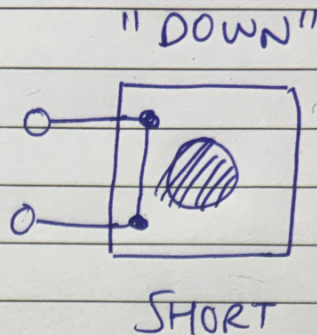
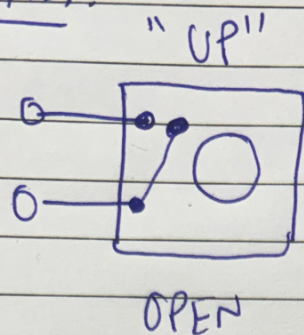


→ Switch:

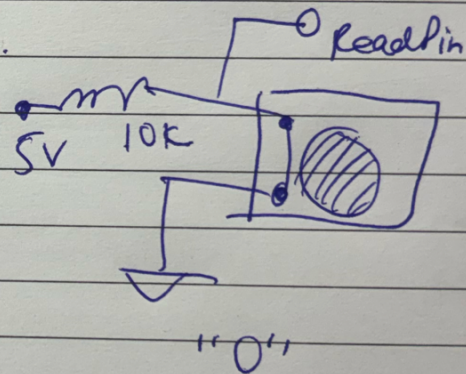

digital read at 5V = 1.
" at 0V = 0.

Pull-up resistor.

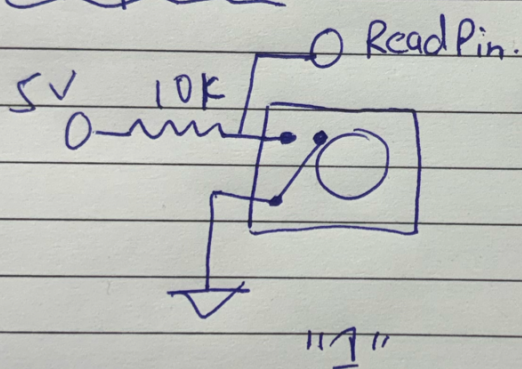

Pull-down resistor

