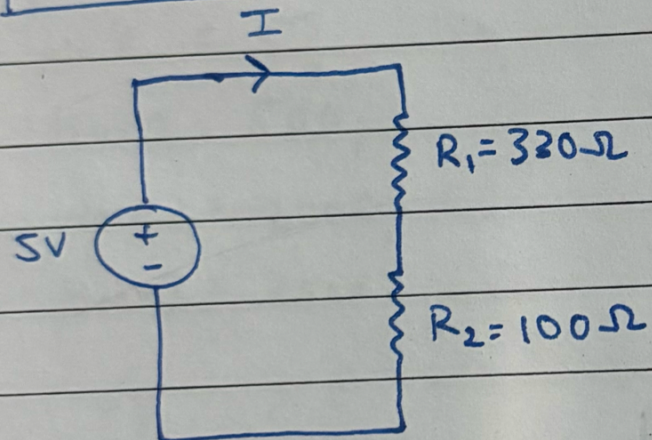


⇒ Ohm's law circuit analysis

$$V = IR$$



$$R_S = R_1 + R_2$$

$$R_S = 430\Omega$$

$$V = IR_S$$

$$I = \frac{5}{430} = 0.011627 \text{ A}$$

$$V_1 = IR_1$$

$$= 11.627 \times 10^{-3} \times 330$$

$$V_1 = 3.83691 \text{ V}$$

$$V_2 = IR_2$$

$$= 11.627 \times 10^{-3} \times 100$$

$$V_2 = 1.16309 \text{ V}$$

$$I = 11.627 \text{ mA}$$