

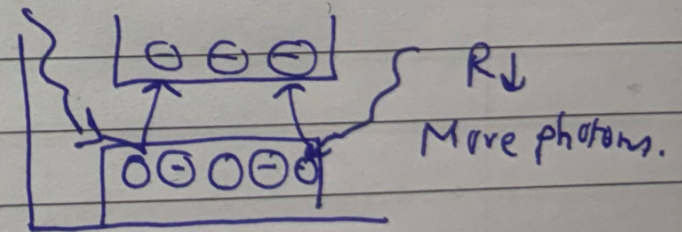
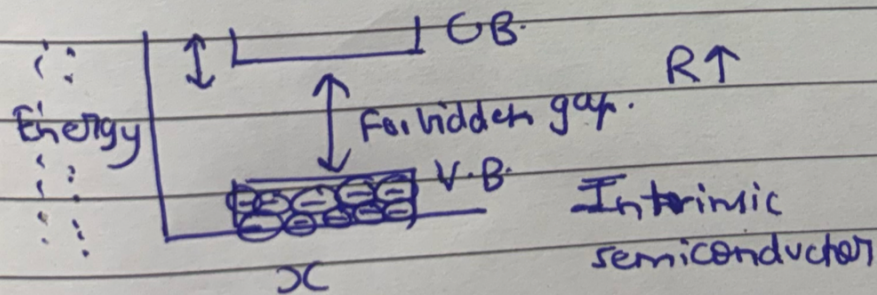


→ Photoresistor

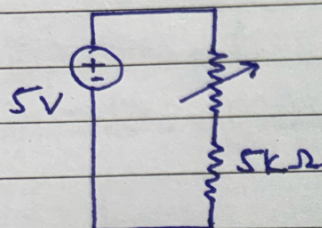Intensity of light
 $L \uparrow, R \downarrow$



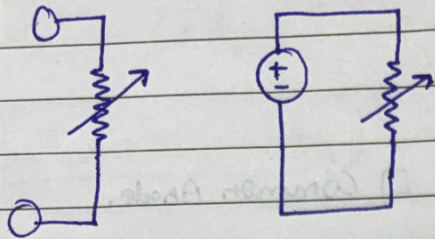• $R_1 = 1.5 \text{ k}\Omega$ when light is very bright.
 $R_2 = 16 \text{ k}\Omega$ when lights are off



$$I = \frac{5}{R_s + 5k}$$


L↑, I↑

L↓, I↓

$$V = \left[\frac{5}{R_s + 5k} \right] \times 5k$$

65, 22

135

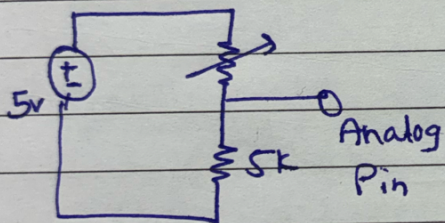

light on :- ~~135~~ 450

light off :- ~~10~~ 355

10

Don't require any other components for this circuit.
Just a 5V source and a 5k resistor.
The output is connected to an Analog Pin.
The output is connected to an Analog Pin.

